

EECT/CE 6325 VLSI DESIGN
Final Project
4-bit Microprocessor

Assignment

You and your partner will design, layout, and simulate a 4-bit calculator that performs the following functions:

- 1) Addition of two 4-bit positive numbers
- 2) Subtraction of two 4-bit positive numbers
- 3) Multiplication of a 4-bit positive number by 2, 4, and 8
- 4) Division of a 4-bit positive number by 2, 4, and 8

This design follows the structure of a finite state machine -- the output of each computation will be used as an input to the next step. The clock is provided externally. The clock signal is a series of voltage pulses, swinging from GND = 0 V to $V_{DD} = 1.2$ V with a 50% duty cycle and 50 ps rise and fall times. The load capacitance connected to the outputs of the calculator is to be 50 fF.

Milestones


- | | |
|---------------|--|
| Due April 2: | Draw a complete block diagram that performs these tasks. (10 points) |
| Due April 9: | Learn to use hierarchical design in schematics and layout. Learn to create a series of signals in HSpice. Draw a floorplan of your calculator. The floorplan includes the estimated geometric positioning of the layouts of different elements that considers continuous power rails (V_{DD} and GND) across different cells and cascading. Submit the floorplan. (10 points) |
| Due April 16: | Design and simulate your transistor-level calculator schematic in Cadence. (20 points) |
| Due April 30: | Finish the layout of your design. Show that a large portion of your schematic passes DRC/LVS. (10 points) |
| Due May 7: | Complete project with simulation of extracted layout. Prepare for a 5-minute class presentation demonstrating functionality, showing metrics, and explaining design choices. (30 points for completion, 20 point design competition) |

Grading

You and your partner will receive the same grade. The final assignment will partially be graded comparatively, with the highest grade going to the group with the lowest area-energy-delay product, *AEDP*, defined as the area of the minimum bounding rectangle that

encloses the full layout multiplied by the minimum possible clock period and the energy consumed to perform a set of testbench operations to be declared on April 30. You must declare what the clock frequency should be for the testing to verify functionality. Each operation is triggered by a positive edge of the clock and finished within one clock cycle. No late assignments will be accepted for any milestone.

Appendix

 

Instruction Set Architecture

INST [1:0] = 00: Addition; ***DATA_OUT [3:0] (n) = DATA_OUT [3:0] (n-1) + DATA_IN [3:0] (n)****

INST [1:0] = 01: Subtraction; ***DATA_OUT [3:0] (n) = DATA_OUT [3:0] (n-1) – DATA_IN [3:0] (n)****

INST [1:0] = 10: Multiplication; ***DATA_IN [2:0] (n) = 100, 010, 001*** means multiplication by 8, 4, 2 on ***DATA_OUT [3:0] (n-1)*, #***

INST [1:0] = 11: Division; ***DATA_IN [2:0] (n) = 100, 010, 001*** means division by 8, 4, 2 on ***DATA_OUT [3:0] (n-1)*, #***

*Neglect the overflow bits

#Multiplication/Division by 000, 011, 101, 110, and 111 is not required

Sample Set of Operations

Reset:	<i>DATA_OUT = 0000</i> [Done with the reset input]	
Operation 1	<i>INST[1:0] = 00, DATA_IN = 0101</i>	<i>DATA_OUT = 0101</i>
Operation 2	<i>INST[1:0] = 01, DATA_IN = 0011</i>	<i>DATA_OUT = 0010</i>
Operation 3	<i>INST[1:0] = 00, DATA_IN = 0001</i>	<i>DATA_OUT = 0011</i>
Operation 4	<i>INST[1:0] = 10, DATA_IN = 0111</i>	<i>DATA_OUT = 0011</i>
Operation 5	<i>INST[1:0] = 10, DATA_IN = 1011</i>	<i>DATA_OUT = 0011</i>
Operation 6	<i>INST[1:0] = 11, DATA_IN = 0011</i>	<i>DATA_OUT = 0011</i>
Operation 7	<i>INST[1:0] = 10, DATA_IN = 0010</i>	<i>DATA_OUT = 1100</i>
Operation 8	<i>INST[1:0] = 11, DATA_IN = 0001</i>	<i>DATA_OUT = 0110</i>

Testing and Verification

DATA_{IN} [3:0] and type/order of operations should be flexible in the design. A list of operations and operands (like the sample one) and the testbench generator script will be posted on April 7.